

LAB-2

TRANSIENT RESPONSE OF SERIES LCR CIRCUIT

[Tejas Kaushik | GUID- 3049840K]

Objective

To study and analyze the transient response of a series LCR circuit, determine the damping constant (α), natural frequency (ω_0), inductance (L), and coil resistance (R_{coil}), and compare experimental and simulated results for under-damped and critically damped conditions.

Milestone 1 – Measurement of Damped Oscillation Period

With $R_{\text{pot}} = 0 \Omega$ and an input of 3 V p-p, the period of the damped oscillations (T_{cd}) was measured using cursors on the oscilloscope. After verifying that the period does not depend on amplitude, the amplitude was reduced to 0.3 V p-p for the rest of the experiment. The average period obtained was:

$$T_{\text{cd}} = 17 \text{ ms}$$

Observation: The oscillation period remained constant across different amplitudes, confirming that the frequency depends on L and C only.


Milestone 2 – Determination of Damping Constant (α), Inductance (L), and Coil Resistance (R_{coil})

Using 0.3 V p-p input and $R_{\text{pot}} = 0 \Omega$, the first two peak amplitudes (O_1 and O_2) of the capacitor voltage were measured from Channel 2 on the oscilloscope.

Measured values: $O_1 = 111.25 \text{ mV}$, $O_2 = 43.7 \text{ mV}$, $T_{\text{cd}} = 12.4 \text{ ms}$.

The damping constant (α) was calculated using the relation: $\alpha = (1/T_{\text{cd}}) \ln(O_1 / O_2) = 75 \text{ s}^{-1}$. From T_{cd} , the damped and natural frequencies were found as $\omega_{\text{cd}} = 506 \text{ rad/s}$ and $\omega_{(0)} = 511 \text{ rad/s}$ respectively. The inductance and coil resistance were then calculated as $L = 3.8 \text{ H}$ and $R_{\text{coil}} = 580 \Omega$.

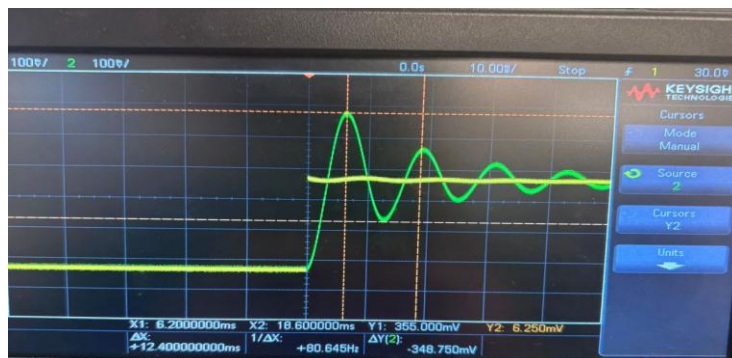Observation: The calculated values confirm that the circuit is under-damped since $\alpha < \omega_0$.




Oscilloscope waveforms showing O_1 and O_2 .

Milestone 3 – Critical Damping

The potentiometer (R_{pot}) was increased gradually until oscillations just disappeared and the output returned to equilibrium without overshoot. This setting represents the critical damping condition.

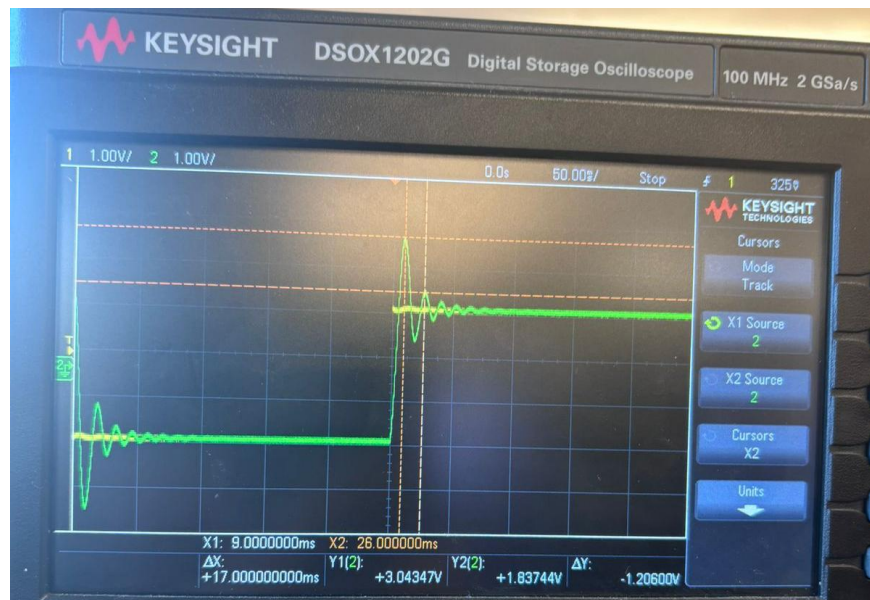The critical resistance was measured as $R_{Cj} = R_{Cpot,critj} + R_{Ccoilj} \approx 3.9 \text{ k}\Omega$, which matches the theoretical value $R_{C,theoryj} = 2\sqrt{L/C} \approx 3.9 \text{ k}\Omega$.



Oscilloscope waveform showing critically damped response.


Milestone 4 – PSpice Simulation

The circuit was simulated in OrCAD/PSpice using VPULSE, R, L, and C components with parameters matching the measured values. Simulations were run for both under-damped ($R = 160 \Omega$) and critically damped ($R = 3.9 \text{ k}\Omega$) cases.


Results:

- $R = 160 \Omega \rightarrow$ Under-damped oscillation observed.
- $R = 3.9 \text{ k}\Omega \rightarrow$ Critically damped response with no overshoot.

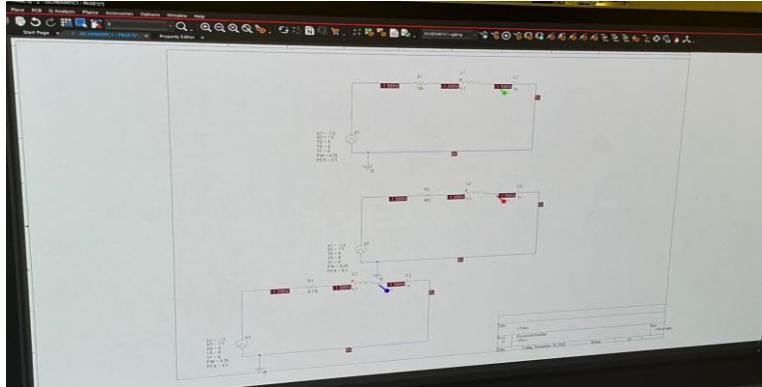The simulated waveforms matched the experimental data closely, confirming theoretical predictions.



PSpice schematic of LCR circuit.

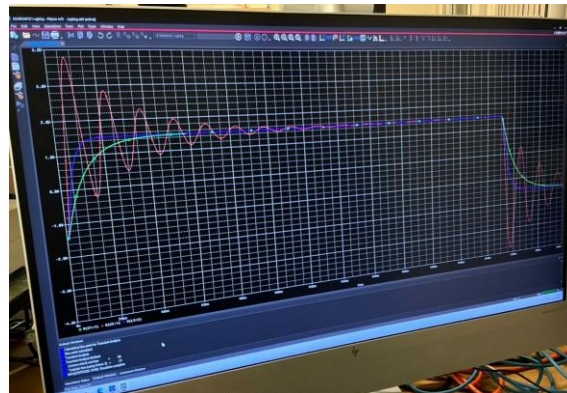

Simulation waveform (under-damped and critically damped).

Conclusion

The transient response of a series LCR circuit was successfully studied. Experimental and simulated results were consistent with theoretical expectations. For $R < R_c$, the circuit was under-damped and exhibited decaying oscillations, while at $R \approx R_c$ the system achieved critical damping. The experiment verified the relationship $R_c = 2\sqrt{L/C}$ and demonstrated how resistance controls the damping behaviour of an LCR circuit.